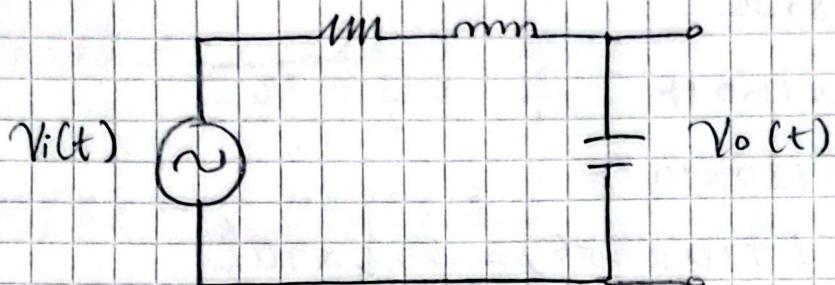


Ejercicio



$$R = 1 \text{ k}\Omega$$

$$L = 180 \text{ mH}$$

$$C = 120 \mu\text{F}$$

1. EDO

$$2. H(\omega) = \frac{Y(\omega)}{X(\omega)} \rightarrow \text{diagrama de Bode [dB]}$$

$$3. H(s) = \frac{Y(s)}{X(s)} \rightarrow \text{diagrama polos y ceros}$$

$$4. h(t) =$$

$$5. y(t) = ?$$

$$H(s) = \frac{V_o(s)}{V_i(s)}$$

$$V_o(s) = V_i(s) \left(\frac{Z_C}{Z_R + Z_L + Z_C} \right)$$

$$Z_R = R$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}}$$

$$Z_L = sL$$

$$Z_C = \frac{1}{sC}$$

$$H(s) = \frac{1}{sCR + s^2 LC + 1}$$

$$H(s) = \frac{1}{LCs^2 + RCS + 1}$$

Cálculo de $h(t)$

$$R = 1 \text{ k}\Omega = 1000 \Omega$$

$$L = 180 \text{ mH} = 0.180 \text{ H}$$

$$C = 120 \mu\text{F} = 120 \times 10^{-6} \text{ F}$$

$$LC = (0.180) \times (120 \times 10^{-6}) = 21.6 \times 10^{-6}$$

$$RC = (1000) \times (120 \times 10^{-6}) = 0.12$$

Entonces

$$H(s) = \frac{1}{21.6 \times 10^{-6}s^2 + 0.12s + 1}$$

$$H(s) = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{4629.63}{s^2 + 0.6666s + 4629.63}$$

Tipo de respuesta

$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

Frecuencia

$$\omega_n^2 = \frac{1}{LC} = 4629.63 \quad \omega_n = \sqrt{4629.63} = 43.04 \text{ rad/s}$$

fáctos

$$2\zeta\omega_n = \frac{R}{L} = \frac{1000}{0.180} = 5555.56$$

$$\frac{RC}{LC} = \frac{R}{L} = \frac{1000}{0.180} = 5555.56$$

$$H(s) = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$H(s) = \frac{1}{LCs^2 + RCs + 1}$$

$$H(s) = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$H(s) = \frac{46296.3}{s^2 + \frac{0.12}{21.6 \times 10^{-6}} s + 4629.63}$$

$$H(s) = \frac{46296.3}{s^2 + 55555.56 s + 4629.63}$$

Comparando con $\frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$

$$\omega_n^2 = 4629.63 \Rightarrow \omega_n \approx 68.04 \text{ rad/s}$$

$$2\zeta\omega_n = 5555.56 \Rightarrow \zeta = \frac{5555.56}{2 \times 68.04} \approx 0.3$$

Cálculo de polos y ceros

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \Rightarrow s^2 + 5555.56s + 4629.63 = 0$$

$$s_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{-5555.56 \pm \sqrt{(5555.56)^2 - 4(4629.63)}}{2}$$

$$s_1 = \frac{-5555.56 + 5553.89}{2} \approx -0.335$$

$$s_2 = \frac{-5555.56 - 5553.89}{2} \approx -5554.725$$

$$H(s) = \frac{46296.3}{(s - s_1)(s - s_2)} = \frac{46296.3}{(s + 0.335)(s + 5554.725)}$$

Fracciones parciales

$$H(s) = \frac{A}{s + 0.335} + \frac{B}{s + 5554.725}$$

$$A = \lim_{s \rightarrow -0.835} (s + 0.835) H(s) = \frac{146296.3}{-0.835 + 5554.725} \approx 8.336$$

$$B = \lim_{s \rightarrow -5554.725} (s + 5554.725) H(s) = \frac{146296.3}{-5554.725 + 0.835} \approx -8.336$$

$$H(s) = \frac{8.336}{s + 0.835} - \frac{8.336}{s + 5554.725}$$

Laplace: $\mathcal{L}^{-1} \left\{ \frac{1}{s+a} \right\} = e^{at} u(t)$

$$h(t) = 8.336 (e^{-0.835t} - e^{-5554.725t}) u(t)$$

Calculo de $y(t)$

$$v_i(t) = u(t)$$

$$v_i(s) = \mathcal{L}\{u(t)\} = \frac{1}{s}$$

La salida en el dominio de Laplace es

$$y(s) = H(s)v_i(s)$$

$$y(s) = H(s) \frac{1}{s} = \frac{1}{s} \left(\frac{8.336}{s + 0.835} - \frac{8.336}{s + 5554.725} \right)$$

$$y(s) = \frac{8.336}{s(s + 0.835)} - \frac{8.336}{s(s + 5554.725)}$$

Fracciones parciales a $\frac{1}{s(s+a)} = \frac{1/a}{s} - \frac{1/a}{s+a}$

$$\text{Para } a_1 = 0.835$$

$$\frac{8.336}{s(s + 0.835)} = 8.336 \left(\frac{1/0.835}{s} - \frac{1/0.835}{s + 0.835} \right) \approx$$

$$8.336 \left(\frac{1.197}{s} - \frac{1.197}{s + 0.835} \right) \approx \frac{10}{s} - \frac{10}{s + 0.835}$$

para $\alpha_2 = 5554.725$

$$\frac{8.336}{s(s+5554.725)} = 8.336 \left(\frac{1/5554.725}{s} - \frac{1/5554.725}{s+5554.725} \right) \approx$$

$$8.336 \left(\frac{0.0018}{s} - \frac{0.0018}{s+5554.725} \right) \approx \frac{0.015}{s} - \frac{0.015}{s+5554.725}$$

$$Y(s) = \frac{A}{s} + \frac{B}{s+s_1} + \frac{C}{s+s_2}$$

$$Y(s) = \frac{1}{s(LCs^2 + RCs + 1)} = \frac{1}{s(21.6 \times 10^{-6}s^2 + 0.72s + 1)}$$

$$A = \lim_{s \rightarrow 0} s Y(s) = \frac{1}{1} = 1$$

$$B = \lim_{s \rightarrow -0.335} (s + 0.335) Y(s) = \frac{1}{(-0.335)(21.6 \times 10^{-6}(-0.335) - 0.72 + 1)} \\ \approx -0.998$$

$$C = \lim_{s \rightarrow 5554.725} (s + 5554.725) Y(s) \approx 0$$

$$Y(s) = \frac{1}{s} + \frac{-0.998}{s + 0.335} + \frac{0.002}{s + 5554.725}$$

transformada inversa de Laplace

$$y(t) = (1 - 0.998 e^{-0.335t} + 0.002 e^{-5554.725t}) u(t)$$

El segundo término exponencial decine muy rápidamente, entonces

$$y(t) \approx (1 - e^{-0.335t}) u(t)$$